

ALTERNATING CURRENT

- A resistance of 20Ω is connected to a source of 110 V, 50 Hz alternating current. Find
 - the rms current
 - the maximum instantaneous current in the resistor and
 - the time taken by current to change from its maximum value to the rms value.

Answer : a) 5.5 A; b) 7.8 A; c) 2.5 ms.

- The electric current in a circuit is given by $i = i_0 \left(\frac{t}{\tau} \right)$ for some time. Calculate the rms current for the period $t = 0$ to $t = \tau$.

Answer : $\frac{i_0}{\sqrt{3}}$

- A capacitor of capacitance $100 \mu\text{F}$ and a coil of resistance 50Ω and inductance 0.5 H are connected in series with a 110 V, 50 Hz ac source. Find the rms value of the current.

Answer : 0.82 A

- A series ac circuit contains an inductor of inductance 20 mH , a capacitor $100 \mu\text{F}$ and a resistance 50Ω . The circuit is connected to ac source of 12 V, 50 Hz. Find the energy dissipated in the circuit in 1000 s.

Answer : 2.3 kJ.

- An electric bulb is designed to consume 55 W when operated at 110 volts. It is connected to a 220 V, 50 Hz line through a choke coil in series. What should be the inductance of the coil for which the bulb gets correct voltage?

Answer :

- In a series LCR circuit with an ac source $R = 300 \Omega$, $C = 20 \mu\text{F}$, $L = 1.0 \text{ Henry}$, $E_{rms} = 50 \text{ V}$ and $f = \frac{50}{\pi} \text{ Hz}$. Find

- the rms current in the circuit and
- the rms potential differences across the capacitor, the resistor and the inductor.

Answer :

- A circuit has a coil of resistance 50Ω and inductance $\frac{3}{\pi} \text{ Henry}$. It is connected in series with a condenser of $\frac{40}{\pi} \mu\text{F}$ and ac supply voltage of 200 V and 50 Hz.

Calculate

- the impedance of the circuit,
- the p.d. across inductance coil and condenser.

Answer :

- An inductor $\frac{2}{\pi} \text{ Henry}$, a capacitor $\frac{100}{\pi} \mu\text{F}$ and a resistor 75Ω are connected in series across a source of emf $V = 10 \sin(100\pi t)$.

- find the impedance of the circuit.
- find the energy dissipated in the circuit in 20 minutes.

Answer :

- A series circuit consists of a resistance, inductance and capacitance. The applied voltage and the current at any instant are given by

$$E = 100\pi \cos(5000t - 10^\circ) \quad \text{and} \quad i = 5 \cos(5000t - 370^\circ)$$

The inductance is 0.01 Henry. Calculate the value of capacitance and resistance.

Answer :

10. An inductance of 2.0 H, a capacitance of $18 \mu\text{F}$ and a resistance of $10 \text{ k}\Omega$ are connected to an ac source of 20 V with adjustable frequency
- What frequency should be chosen to maximise the current (rms) in the circuit?
 - What is the value of this maximum current (rms)?

Answer :

11. An inductor-coil a capacitor and an ac source of rms voltage 24 V are connected in series. When the frequency of the source is varied a maximum rms current of 6.0 A is observed. If this inductor coil is connected to a battery of emf 12 V and internal resistance 4.0Ω , what will be energy stored in the inductor?

Answer :

12. A wave of wavelength 300 metre can be transmitted by a transmission centre. A condenser of capacity $2.5 \mu\text{F}$ is available. Calculate the inductance of the required coil for a resonant circuit. (Take $\pi = \sqrt{10}$).

Answer :

13. A coil has a resistance of 10Ω and an inductance of 0.4 H. It is connected to an ac source of 6.5 V, 60 rad/s. Find the average power consumed in the circuit.

Answer : $\frac{5}{8} \text{ W}$.

14. An electric bulb is designed to consume 55 W when operated at 110 V. It is connected to a 220 V, 50 Hz line through a choke coil in series. What should be the inductance of the coil for which the bulb gets correct voltage?

Answer : 1.2 H

15. In a series LCR circuit with $R = 300 \Omega$, $C = 20 \mu\text{F}$ and $L = 1 \text{ H}$ is connected to an ac source of 50 V, 100 rad/s. Find
- the rms current in the circuit,
 - the rms value of potential difference across the capacitor, resistor and inductor
 - average electric field energy stored in the capacitor
 - average magnetic field energy stored in the inductor

Answer : a) 0.1 A; b) 50 V, 30V, 10 V; c) 25 mJ, 5 mJ

16. An inductor coil a capacitor and an ac source of variable frequency and rms voltage 24 V are connected in series. When frequency of the source is varied a maximum rms current of 6.0 A is observed. If this inductor coil is connected to a battery of emf 12 V and internal resistance 4Ω , what current will flow through the coil?

Answer : 1.5 A.

17. 200 km long telegraph wire has a capacity of $0.014 \mu\text{F}/\text{km}$. If it carries an alternating current of 5,000 Hz, find the inductance of an inductor required to be connected in series for the minimum impedance of the line.

Answer : $360 \mu\text{H}$.

18. A 100 V ac source of frequency 500 Hz is connected to a LCR circuit with $L = 8.1 \text{ mH}$, $C = 12.5 \mu\text{F}$ and $R = 10 \Omega$, all connected in series. Find the potential difference across the resistance.

Answer : 100 V.

19. A series LCR circuit with 100Ω resistance is connected to an ac source of 200 V and angular frequency 300 rad/s. When only capacitance is removed, the current lags behind voltage by 60° , when only inductance is removed, the current leads voltage by 60° . Calculate the current in LCR circuit. Also find the power dissipated in the circuit.

Answer : 2 amp, 400 W.

20. A current of 4 A flows in a coil when connected to a 12 V dc source. If the same coil is connected to a 12 V, 50 rad/s ac source, a current of 2.4 amp flows in the

circuit. Determine the inductance of the coil. Also find the power developed in the circuit if a 2.5 mF capacitor is connected in series with the coil.

Answer : 80 mH, 17.28 W.

21. A LCR circuit has $L = 10$ mH, $R = 3 \Omega$ and $C = 1 \mu\text{F}$ connected in series to a source of $V = 15 \cos(\omega t)$ volts. Calculate the current amplitude and average power dissipated per cycle at a frequency that is 10% lower than the resonant frequency.

Answer : 0.7 amp, 0.74 W.

22. The current in an ideal coil of self inductance 2.0 H is increasing according to $i = 2 \sin t^2$ amp. Find the amount of energy spent by source during the period when the current changes from zero to 2 amp.


Answer : 4 J.

23. A 750 Hz, 20 V source is connected to a resistance of 100 Ω , an inductance of 0.1803 H and a capacitance of 10 μF all in series. Calculate the time in which the resistance (thermal capacity = 2 J/ $^\circ\text{C}$) will get heated by 10 $^\circ\text{C}$.

Answer : 348 s.

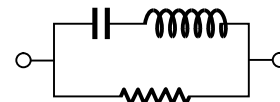24. A box contains L , C and R . When 250 V dc is applied to the terminals of the box, a current of 1.0 amp, flows in the circuit. When an ac source of 250 V rms at 2250 rad/s is connected, a current of 1.25 amp rms flows. It is observed that the current rises with frequency and becomes maximum at 4500 rad/s. Find the values of L , C and R . Also draw the circuit diagram.

Answer : $\frac{4}{81}$ H, 1 μF , 250 Ω ,



25. A series LCR circuit containing a resistance of 120 Ω has angular frequency of resonance as 4×10^5 rad/s. At resonance the voltage across resistance and inductor are 60 V and 40 V respectively. Find the value of L and C . At what frequency the current in the circuit lags the voltage by 45 $^\circ$?

Answer : 0.2 mH, $\frac{1}{32}$ μF , 8×10^5 rad/s.

26. A choke coil is needed to operate an arc lamp at 160 V (rms) and 50 Hz. The arc lamp has an effective resistance of 5 Ω when running at 10 A (rms). Calculate the inductance of the choke coil. If the same arc lamp is to be operated on 160 V dc, find the additional resistance is required to be connected in series. Find the % loss of power in dc circuit.

Answer : 50 mH, 11 Ω , 68.75 %

27. A box P and a coil Q are connected in series with an ac source of variable frequency. The emf of source is constant at 10 V. Box P contains a capacitance of 1 μF in series with a resistance of 32 Ω . Coil Q has a self inductance 4.9 mH and a resistance of 68 Ω . The frequency of source is adjusted so that the maximum current flows in P and Q . Find the impedance of P and Q at this frequency. Also find the voltage across P and Q respectively.

Answer : 76 Ω , 98 Ω , 7.6 V, 9.8 V.

28. An inductor 20 mH, a capacitor 100 μF and a resistor 50 Ω are connected in series across a source of emf $V = 10 \sin(100\pi t)$. Find the energy dissipated in the circuit in 20 minute. If resistance is removed from the circuit and the value of inductance is doubled, then find the current as a function of time in the new circuit.

Answer : 952 J, $i = 0.52 \cos(100\pi t)$

29. In a series resonance LC circuit of resonance frequency 20 k Hz, the inductance of the inductor is π m H. Find the current through the circuit if an ac voltage 90 V, 10 k Hz is applied to it. (Take $\pi = \sqrt{10}$)

Answer : 0.15 amp

30. 250 V, 100 W bulb is to be operated by a 300 V ac supply. Find the series resistance required for the proper operation of the bulb. When the resistance is replaced by an inductor of inductance of $\frac{50}{\pi}$ mH, the bulb still operates properly.


Find the frequency of the ac source. Also find the percentage saving on power in replacing resistance by inductor.

Answer : 125 Ω , 4146 Hz, $\frac{50}{3}$ %

31. The power factor of an LR circuit connected across 240 V, 50 Hz ac power supply is 0.6. Circuit generates 120 W of heat. Find the capacitance required to be connected in series to change the power factor to unity. What is the new rate of generation of heat.

Answer : 13.8 μF , $\frac{1000}{3}$ W

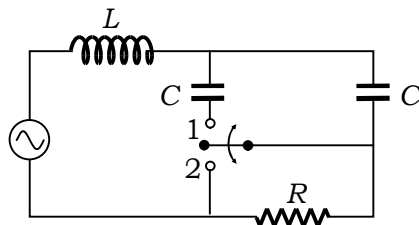32. The ac generator in figure supplies 150 V_(max) at 50 Hz. With the switch open as in the diagram, the resulting current leads the generator emf by 60°. With the switch in position 1, the current lags the generator emf by 30°. When the switch is in position 2, the maximum current is 3 A. Then the value of R is



Answer :